Introduction to series and parallel circuits


Aim

To compare series and parallel circuits

Equipment or Apparatus:

A power pack
Connecting wires
Three lights
NOTE: When using the Power pack you must use DC= direct current

Series Circuits

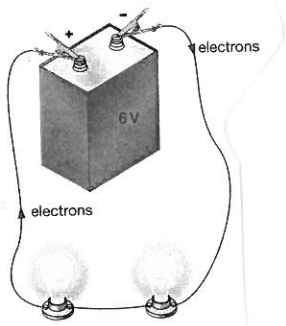

1. Construct a series circuit like in the diagram using two light bulbs
2. Now construct another series circuit using one bulb.

Q1 How does the brightness of two bulbs compare with using one bulb?

_____

_____

Q2 What is the effect of removing one bulb?

_____

_____

Q3 Predict what would happen if 3 bulbs were added to the circuit.

_____


_____

Q4 Would it be sensible to have the lights in your home connected in series?

_____

_____

Parallel Circuits

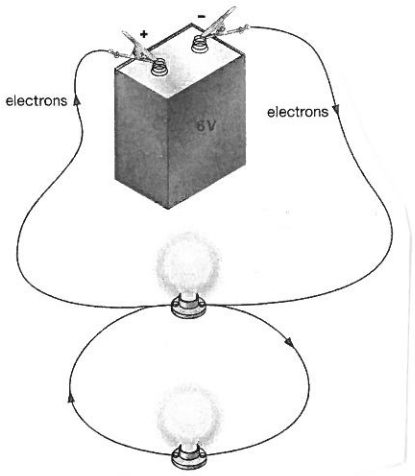

1. Connect a parallel circuit like in the diagram using two bulbs
2. Now construct another circuit using 3 bulbs

Q1 How does the brightness of two bulbs compare with using three bulbs?

Q2 What is the effect of removing one bulb? Does it matter which bulb is removed?

Q3 Would it be better to have the lights in your home connected in series or parallel?